

POWER IN: J1 power only (D+/D− not fitted). Q1 cut (on by default), U2 ideal diode onto the XIAO's 5V

U2 ~CE tied to VOUT: the datasheet's ideal-diode mode (blocks current back into J1). The XIAO's 5V pin IS its USB-C VBUS (no part between, Seeed v1.2 schematic): a computer on the XIAO port and a charger on J1 share +5V. Firmware pulls PWR_CUT low once a computer has enumerated it (device mode): Q2 off, Q1 off, J1 cut. At reset PWR_CUT floats: R4/R5 hold Q2 on, so a charger alone always starts it.
C4 (100 uF) not fitted: host-mode hot-plug reserve, against USB's 10 uF limit for a device.

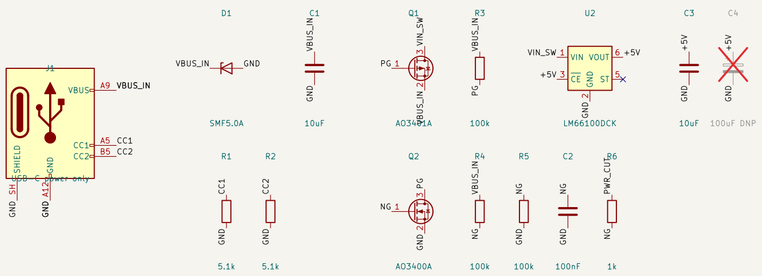


XIAO ESP32S3 (Seeed footprint, 2 x 7 headers or castellations)

D6 = GPIO43 has 499 ohm on the module (U0TXD). D2 = GPIO3 strapping, ignored by default eFuses. ENC_A = D6 = GPIO43, ENC_B = D7 = GPIO44 (U0TXD / U0RXD), IN_EN = D4 = GPIO5, MIDI_RX = D5 = GPIO6 (v5).
v5: MIDI_TX1 = D0 = GPIO1 (OUT1 alone; Hi-Z in IN mode); MIDI_TXB = D1 = GPIO2 drives OUT2, OUT3 and OUT4 together (3 loops on one pad).
LADDER = D2 = GPIO3 (ADC1): OK / BACK / PUSH on one resistor ladder. LED_DATA = D3 = GPIO4, SCL = D8 = GPIO7, SDA = D9 = GPIO8 (the OLED, I2C by the GPIO matrix). PWR_CUT = D10 = GPIO9, low = J1 cut.

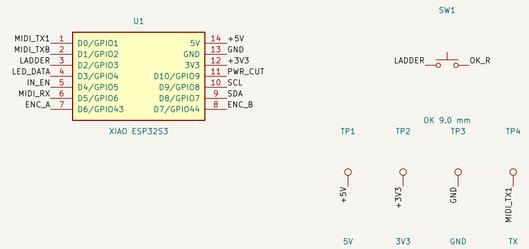

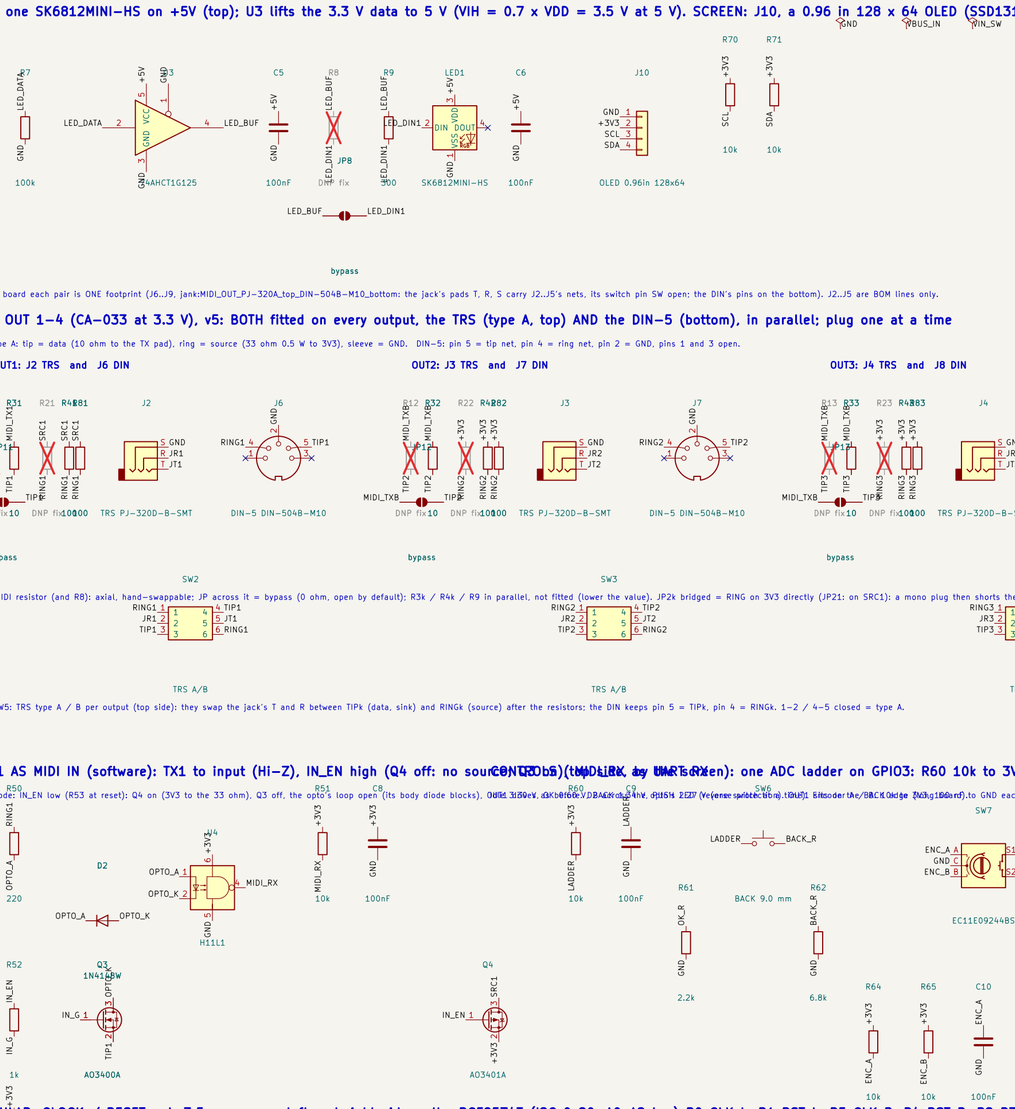LED: one SK6812MINI-HS on +5V (top); U3 lifts the 3.3 V data to 5 V (VIH = 0.7 x VDD = 3.5 V at 5 V). SCREEN: J10, a 0.96 in 128 x 64 OLED (SSD1315, I2C 0x3C, 3V3)




On the board each pair is ONE footprint (J6..J9, jank:MIDI_OUT_PJ-320A_top_DIN-504B-M10_bottom: the jack's pads T, R, S carry J2..J5's nets, its switch pin SW open; the DIN's pins on the bottom). J2..J5 are BOM lines only.

MIDI OUT 1-4 (CA-033 at 3.3 V), v5: BOTH fitted on every output, the TRS (type A, top) AND the DIN-5 (bottom), in parallel; plug one at a time


TRS type A: tip = data (10 ohm to the TX pad), ring = source (33 ohm 0.5 W to 3V3), sleeve = GND. DIN-5: pin 5 = tip net, pin 4 = ring net, pin 2 = GND, pins 1 and 3 open.

OUT1: J2 TRS and J6 DIN

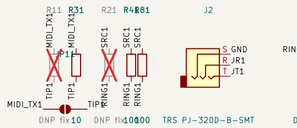


OUT2: J3 TRS and J7 DIN

OUT3: J4 TRS and J8 DIN

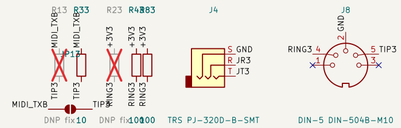


OUT4: J5 TRS and J9 DIN

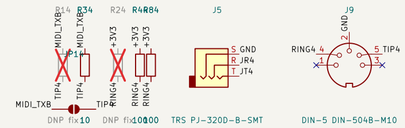

bypass

SW2 SW3 SW4 SW5

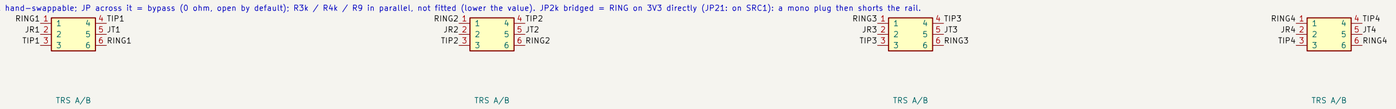
Each MIDI resistor (and R8): axial, hand-swappable; JP across it = bypass (0 ohm, open by default): R3k / R4k / R9 in parallel, not fitted (lower the value). JP2k bridged = RING on 3V3 directly (JP21: on SRC1): a mono plug then shorts the rail.



SW2..SW5: TRS type A / B per output (top side): they swap the jack's T and R between TIPk (data, sink) and RINGk (source) after the resistors; the DIN keeps pin 5 = TIPk, pin 4 = RINGk. 1-2 / 4-5 closed = type A.

OUT1 AS MIDI IN (software): TX1 to input (Hi-Z), IN_EN high (Q4 off: no source on TX1), MIDI_RX to UART RX (open): one ADC ladder on GPIO3: R60 10k to 3V3; OK 2.2k, BACK 6.8k, PUSH 22k to GND each.

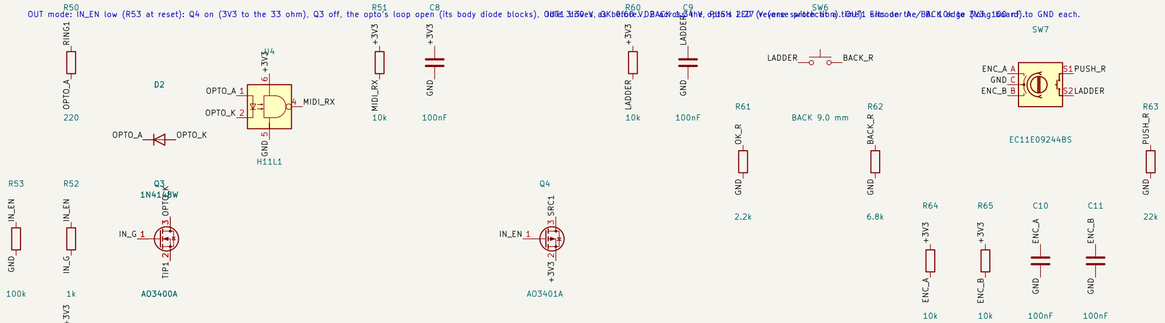OUT mode: IN_EN low (R53 at reset): Q4 on (3V3 to the 33 ohm), Q3 off, the opto is loop open (its body diode blocks). OUT1 is now a receiver, MIDI_RX (GPIO6) listens to it. Switch the BACK edge (2.2k) to GND each.



MODULAR: CLOCK / RESET out, 3.5 mm mono, left and right side walls: PCF8574T (I2C 0x20, A0..A2 low) P0 CLK_L, P1 RST_L, P5 CLK_R, P4 RST_R; P2 P3 P6 P7 spare on TP5..TP8

generated by make_schematic.py: do not edit by hand
hardware/pcb/README.md: the power path, the pin table and every unverified item

Sheet: /
File: jank-pcb-mod.kicad_sch

Title: jank: XIAO ESP32S3 MIDI clock stick

Size: A2	Date: 2026-11-08	Rev: 0.1 schematic for review
KiCad E.D.A. 10.0.8		Id: 1/1